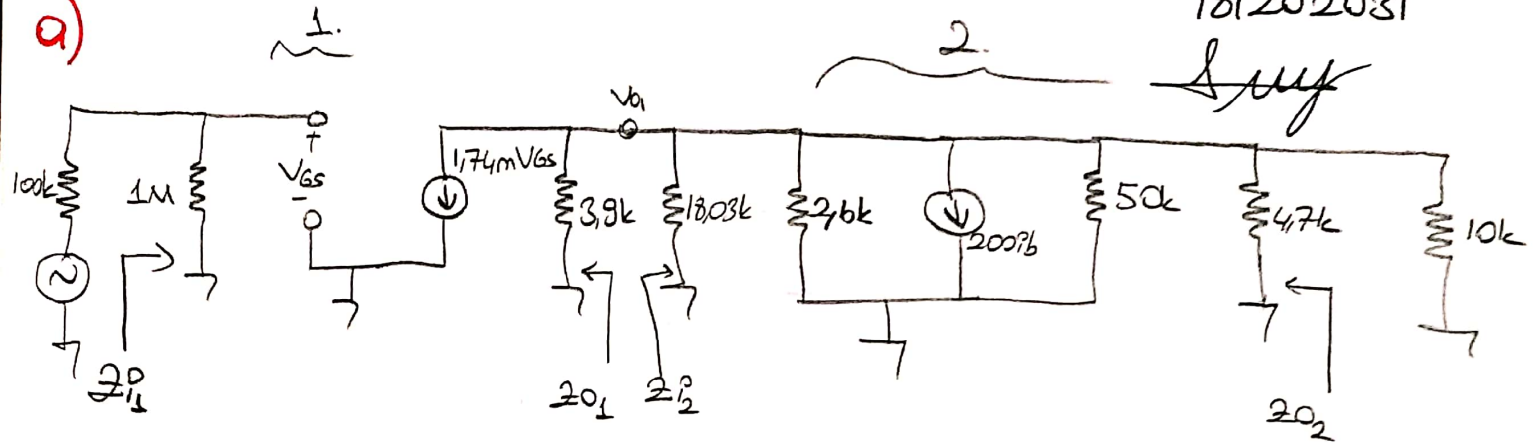


Soru ①

Fatih Furkan ERDOY

18/202031

a)



$$I_G \cdot 1M + V_{GS} + 1.5k \cdot I_D = 0 \quad -1.5k I_D = V_{GS} \Rightarrow I_D = 6m \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\Rightarrow \frac{-V_{GS}}{1.5k} = 6m \left(1 + \frac{V_{GS}}{3}\right)^2 \Rightarrow -V_{GS} = 9 \left(1 + \frac{2V_{GS}}{3} + \frac{V_{GS}^2}{9}\right) \Rightarrow -V_{GS} = 9 + 6V_{GS} + V_{GS}^2$$


$$\Rightarrow V_{GS}^2 + 7V_{GS} + 9 = 0$$

$$V_{GS1} = \frac{-7 + \sqrt{13}}{2} = -1.697V \quad V_{GS2} = \frac{-7 - \sqrt{13}}{2} = -5.302$$

$$V_{GS} < V_P \text{ olacağı için } \boxed{V_{GS} = -1.697}$$

$$g_m = \frac{2I_{DSS}}{|V_P|} \cdot \left(1 - \frac{V_{GS}}{V_P}\right) \quad g_m = \frac{12m}{3} \cdot \left(1 - \frac{(-1.697)}{(-3)}\right) = \boxed{g_m = 1.737mS}$$
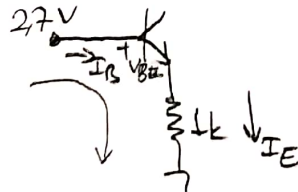
$$V_B = \frac{15 \cdot 22k}{122k} = 2.7V$$



$$\Rightarrow 2.7 - V_{BE} - I_E \cdot 1k = 0$$

$$2.7 - 0.7 = I_E \cdot 1k$$

$$\boxed{I_E = 2mA} \approx \boxed{I_{CQ} = 2mA}$$

$$r_e = \frac{26mV}{I_{CQ}} = \frac{26mV}{2mA} = 13\Omega \quad h_{ie} = \beta \cdot r_e \Rightarrow 200 \cdot 13 = 2.6k$$

$$\boxed{h_{ie} = 2.6k}$$

$$\boxed{Z_{i1} = 1M\Omega}$$

$$Z_{i2} = 100k // 22k // 2.6k$$

$$\boxed{Z_{i2} = 2.27k\Omega} \quad Z_{o2} = 4.7k // 50k$$

$$\boxed{Z_{o1} = 3.9k\Omega} \quad \boxed{Z_{o2} = 4.29k\Omega}$$

$$A_{V1} = -g_m (R_D // Z_{i2}) = -1.734 (3.9k // 2.27k) = \boxed{A_{V1} = -2.492}$$

$$A_{V2} = \frac{-h_{fe}}{h_{ie}} (R_C // R_L // 50k) = \frac{-200}{2.6k} (4.7k // 10k // 50k) = \boxed{A_{V2} = -231.143}$$

$$A_V = A_{V1} \cdot A_{V2} \Rightarrow -2.492 \cdot -231.143 = 576.008$$

$$\boxed{A_V = 576.008}$$

Soru (1) - Devamı

Fatih Furkan ERSOY
181202031

1 say

$$b) C_{C1} = \frac{1}{2 \cdot \pi \cdot f \cdot (R_g + R_G)} = \frac{1}{2 \cdot \pi \cdot 10 \cdot (1M + 100k)} = 0,014 \mu F$$

$$C_{C2} = \frac{1}{2 \pi f (R_D + R_{i2}')} = \frac{1}{2 \pi 10 (3,9k + 2,27k)} = 2,579 \mu F$$

$$C_{C3} = \frac{1}{2 \pi f (Z_{O2} + R_g)} = \frac{1}{2 \pi \cdot 10 (4,29k + 10k)} = 1,113 \mu F$$

c) FET

$$C_{in} = C_{gs} + C_{gd}(1 - A_{V1}) + C_{w1} \Rightarrow 13,476 pF = 3 pF + 3 pF(1 + 2,492) + 0$$

$$R_{in} = 100k // 1M$$

$$R_{in} = 90,9k \Omega$$

$$f_{Cin} = \frac{1}{2 \cdot \pi \cdot 13,476 \cdot 10^{-12} \cdot 90,9 \cdot 10^3} = 129,93 k Hz$$

$$C_{out} = C_{ds} + C_{gd}\left(1 - \frac{1}{A_{V1}}\right) + C_{w2} \Rightarrow 5,2 pF = 1 pF + 3 pF\left(1 + \frac{1}{2,492}\right) + 0$$

$$f_{Cout} = \frac{1}{2 \pi \cdot 5,2 \cdot 10^{-12} \cdot 1,435 \cdot 10^3} = 21,3 MHz$$

$$R_{out} = 3,9k // 2,27k$$

$$R_{out} = 1,435k \Omega$$

BJT

$$C_{in} = C_{be} + C_{bc} \cdot (1 - A_{V2}) + C_{w1} \Rightarrow 776,75 pF = 80 pF + 3 pF(1 + 231,15) + 0$$

$$R_{in} = 1,43k \Omega$$

$$f_{Cin} = \frac{1}{2 \pi \cdot 776,75 \cdot 10^{-12} \cdot 1,435 \cdot 10^3} = 143,3 k Hz$$

$$C_{out} = C_{ce} + C_{bc}\left(1 - \frac{1}{A_{V2}}\right) + C_{w2} \Rightarrow 9,01 pF = 6 pF + 3 pF\left(1 + \frac{1}{231,15}\right) + 0$$

$$R_{out} = 3,9k // 2,27k$$

$$R_{out} = 1,435k \Omega$$


$$f_{Cout} = \frac{1}{2 \pi \cdot 9,013 \cdot 10^{-12} \cdot 3.005 \cdot 10^3} = 5,876 MHz$$

$$f_{üst+min}(f_{Cin}, f_{Cout}, f_{Cin2}, f_{Cout2}) = \boxed{f_{üst+min} = 129,93 k Hz}$$

Soru (2)

Fatih Furkan ERSOY
181202031

Sunay

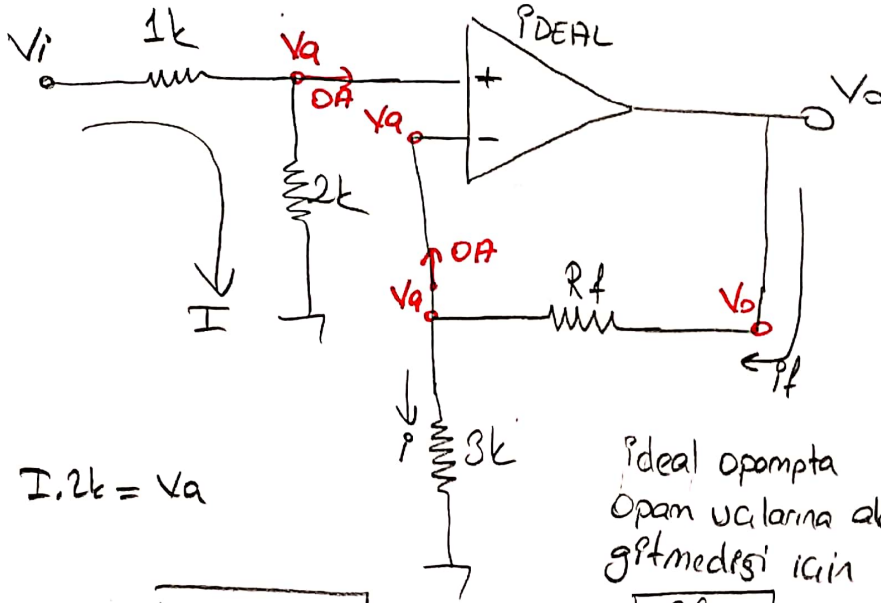

Kazancın 5 olması
Pcin Rf

$$\boxed{\frac{V_o}{V_i} = 5 \text{ pcin}} \quad \text{Pcin}$$

V_a

$$\frac{V_i}{3k} = I \quad I \cdot 2k = V_a$$

$$\frac{V_i}{3k} \cdot 2k = V_a \Rightarrow \boxed{V_a = \frac{2}{3} V_i}$$

İdeal opampta
Opam uçlarına akım
girmemesi için

$$\boxed{I_f = I} \text{ olur}$$

Bu eşitliği kullanırsak,

$$\frac{V_o - V_a}{R_f} = \frac{V_a - 0}{3k} \Rightarrow 3k \cdot (V_o - V_a) = V_a \cdot R_f$$

$$\Rightarrow \boxed{V_o = 5V_i} \rightarrow \text{kazanca}$$

$$\Rightarrow 3k \left(V_o - \frac{2V_i}{3} \right) = \frac{2V_i}{3} \cdot R_f$$

$$\Rightarrow 3k \cdot \left(5V_i - \frac{2V_i}{3} \right) = \frac{2V_i}{3} \cdot R_f$$

$$\Rightarrow 45k V_i - 6k V_i = 2V_i R_f$$


$$\Rightarrow 39k V_i = 2V_i R_f$$

$$\frac{39k}{2} = R_f$$

$$\boxed{R_f = 19,5k}$$

Soru (3)

Fatih Furkan ERSOY
181202031
1 May

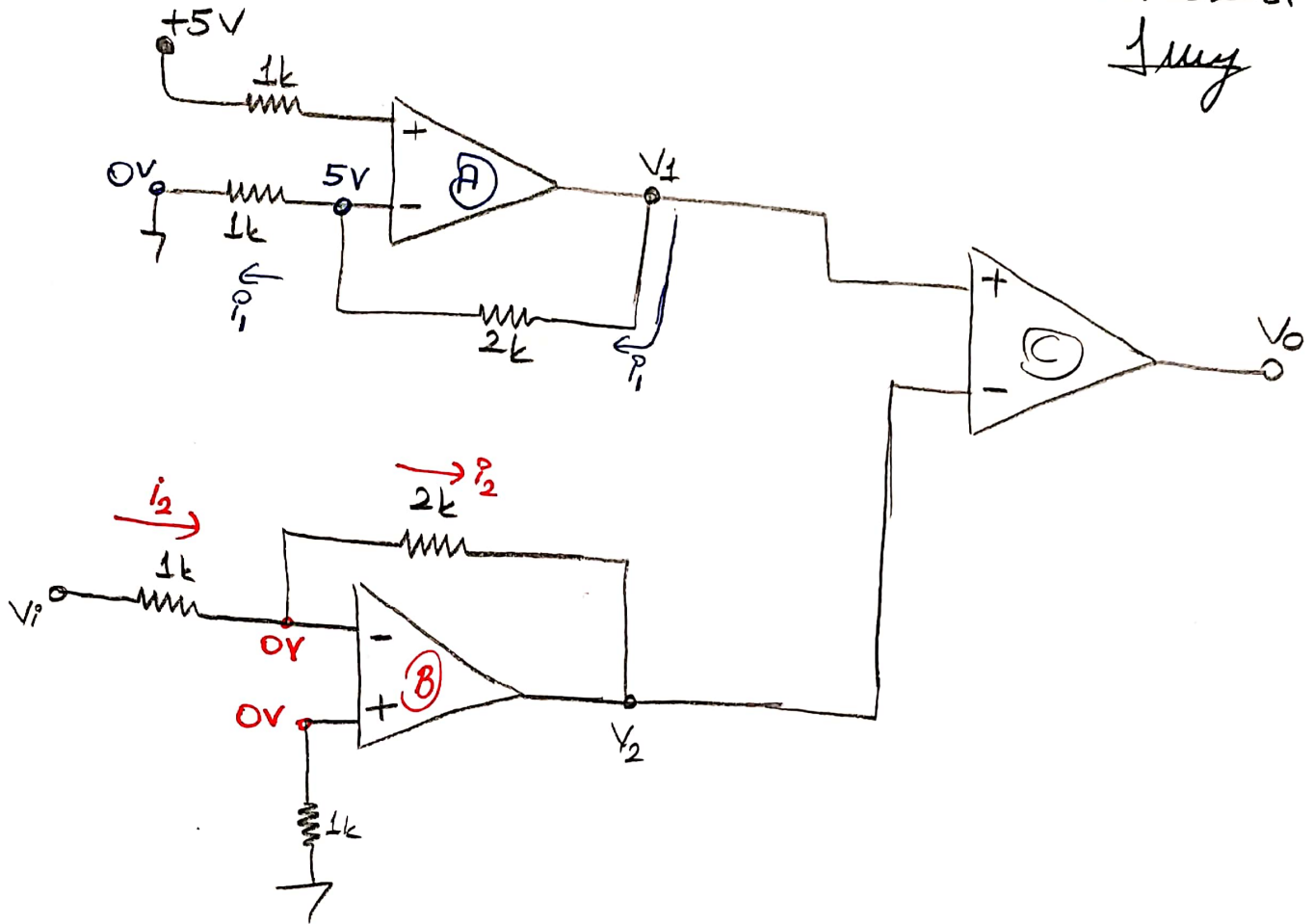

(A)

$$\frac{5-0}{1k} = \frac{V_1-5V}{2k} \Rightarrow 10 = V_1-5V \quad \boxed{V_1=15V} \text{ ama } V_{cc} = \pm 6V \text{ old. i\u00e7in}$$

$$\boxed{V_1=6V}$$

(B)

$$\frac{V_i-0}{1k} = \frac{0-V_2}{2k} \Rightarrow 2V_i = -V_2 \Rightarrow \boxed{V_2 = \pm 2V(\sin'in \text{ tersi})}$$





(C)

$$V_1 > V_2 \text{ old. i\u00e7in}$$

$$\boxed{V_0=6V}$$

Soru(3) - Devamı

Fatih Furkan ERsoy
181202031
İmy

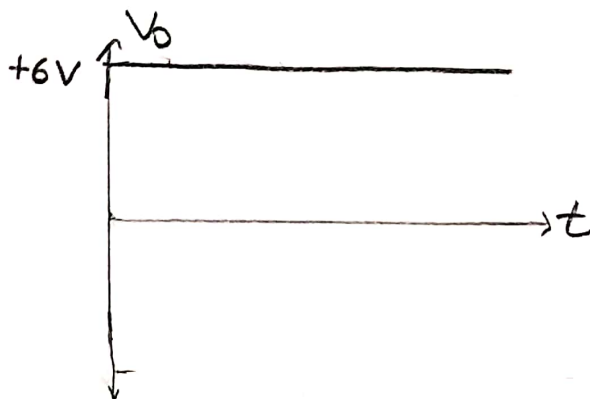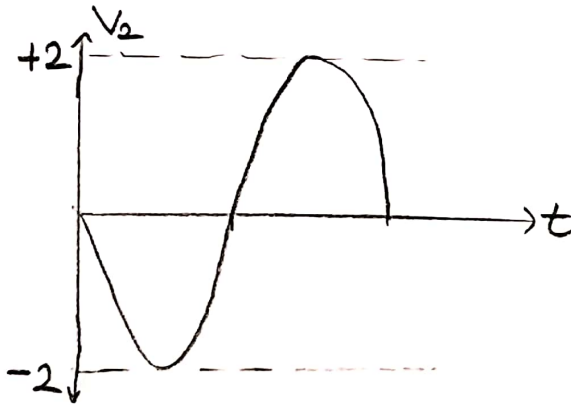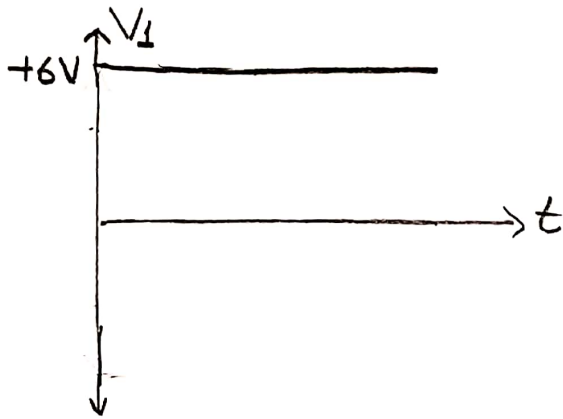
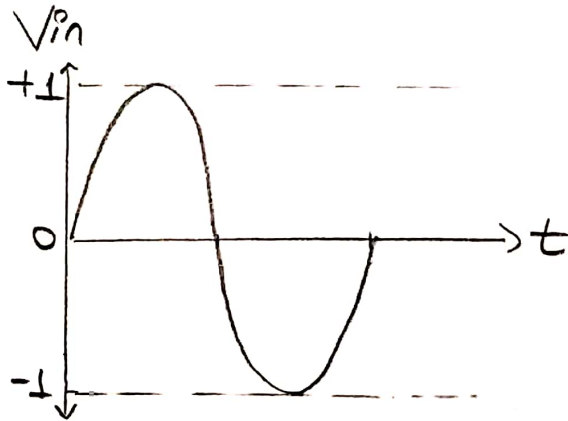


Soru (4)

Fatih Furkan ERSOY

181202031

İmza

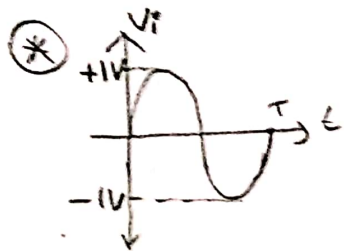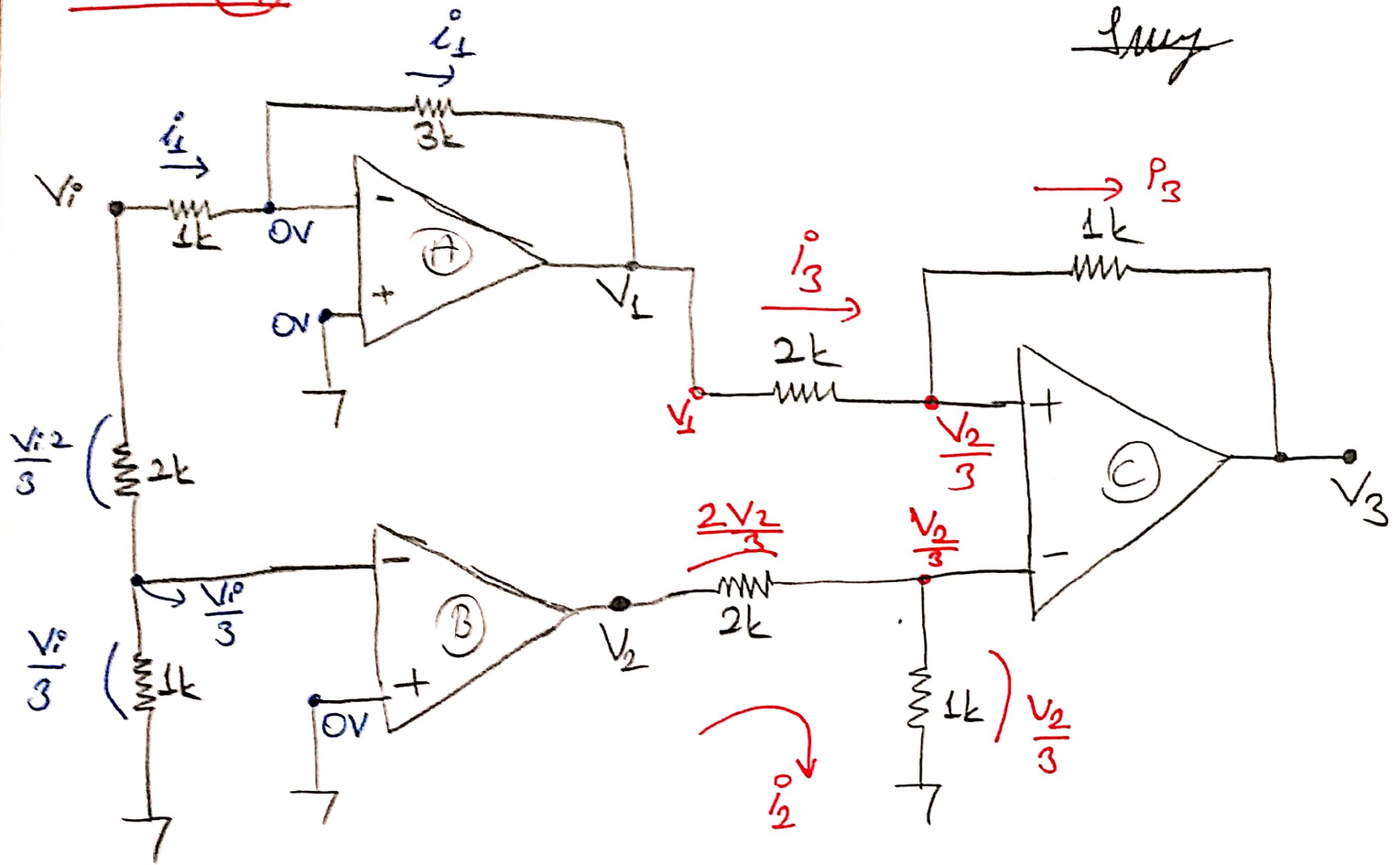

$$V_{CC} = \pm 12V$$

(A) Opamp1

$$i_1 = \frac{V_p - 0}{1k} = \frac{0 - V_1}{3k} \Rightarrow 3V_p = -V_1$$

(B) Opamp1

$$\left. \begin{array}{l} \frac{V_p}{3} \\ 0V \end{array} \right\} V_2 = \left[\begin{array}{l} \frac{V_p}{3} > 0V \rightarrow +12V \\ \frac{V_p}{3} < 0V \rightarrow -12V \\ 0V \rightarrow 0V \end{array} \right]$$

(C) Opamp1

$$i_3 = \frac{V_1 - \frac{V_2}{3}}{2k} = \frac{\frac{V_2}{3} - V_3}{1k}$$

$$i_3 = V_1 - \frac{V_2}{3} = \frac{2}{3}V_2 - 2V_3$$

$$i_3 = 2V_3 = \frac{2V_2}{3} + \frac{V_2}{3} - V_1$$

$$i_3 = V_3 = \frac{V_2 - V_1}{2}$$

Soru(4) - Devamı

Fatih Furkan ERSOY

181202031

1 May

