
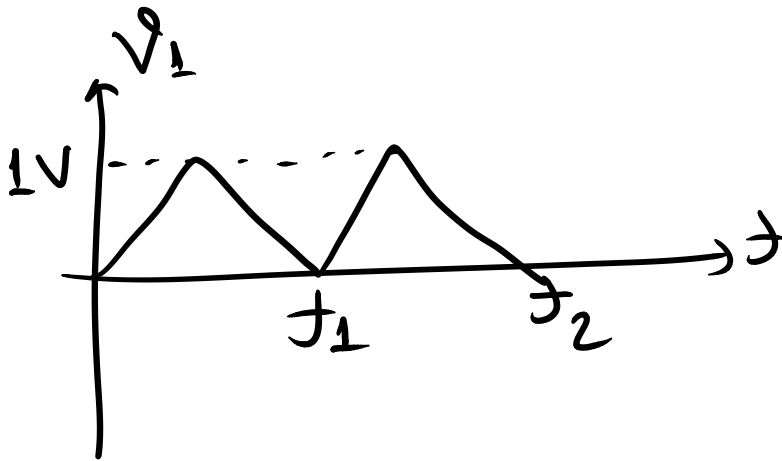


Karışık Örnekler

Örnek-1:

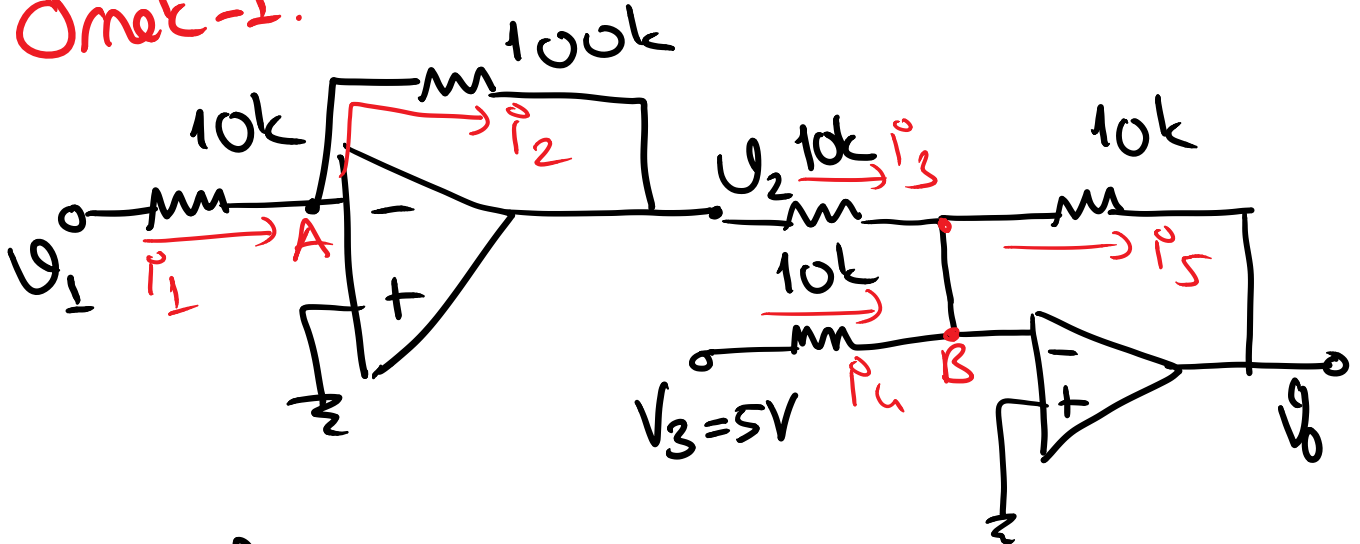

$$\pm V_{cc} = \pm 12V$$

* 1. op-amp'ta .

$$i_1 = i_2$$

$$\frac{V_1}{10k} = -\frac{V_2}{100k}$$

$$\left. \begin{array}{l} i_1 = i_2 \\ \frac{V_1}{10k} = -\frac{V_2}{100k} \end{array} \right\} \boxed{V_2 = -10V_1}$$

* 2. op-amp'ta.


$$i_3 + i_4 = i_5$$

$$\frac{V_2}{10k} + \frac{5}{10k} = -\frac{V_0}{10k} \Rightarrow$$


$$V_0 = -(V_2 + 5)$$

Çizim:


● V_2 'nin çizimi

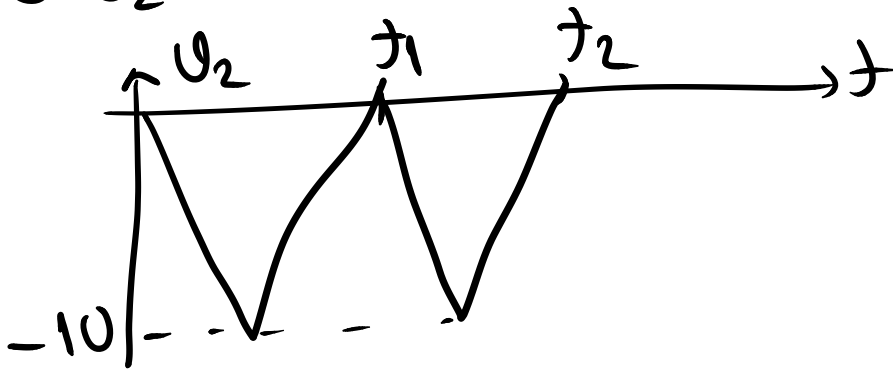



● V_0 'nin çizimi:

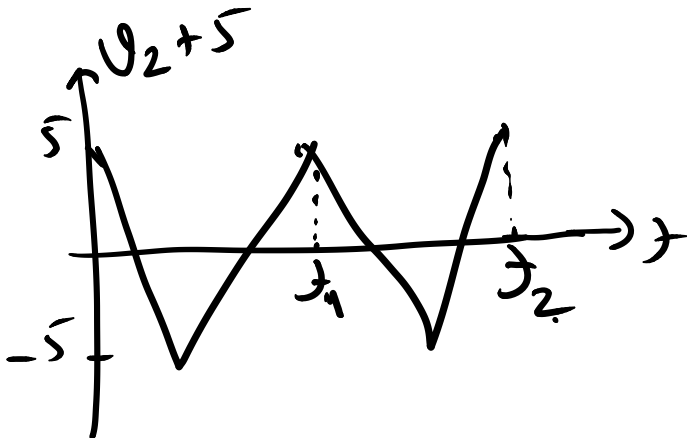


$$V_0 = -(V_2 + 5)$$

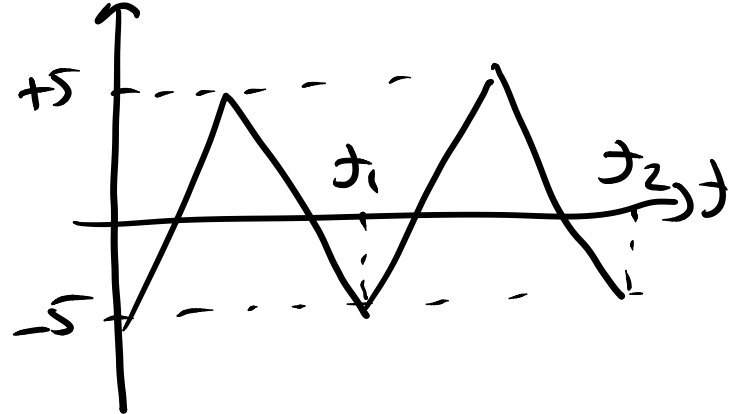

Örnek-2:

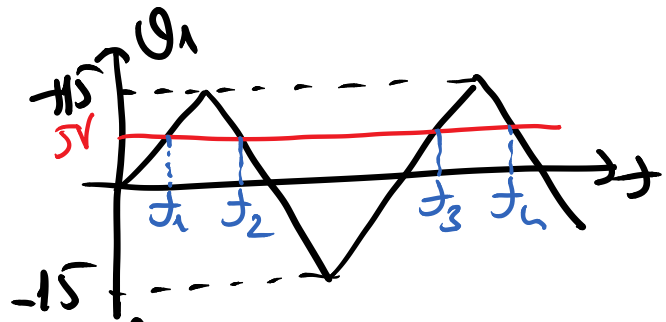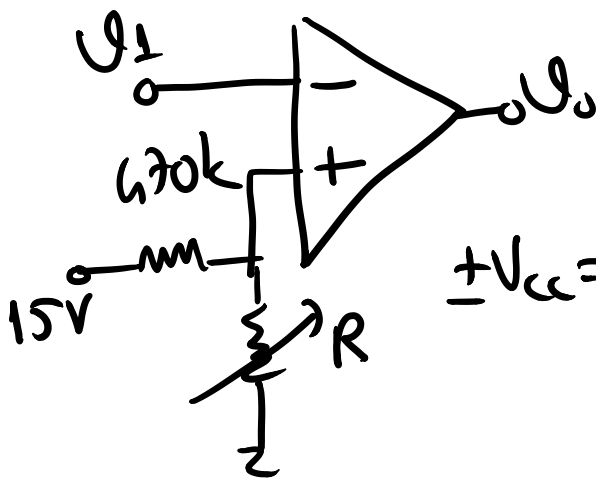

$$\pm V_{cc} = \pm 12V$$

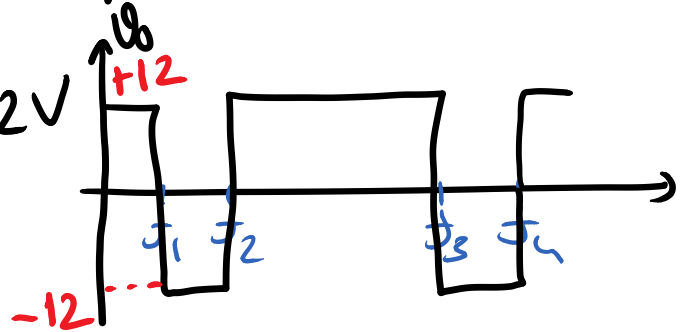


$$R = ?$$

$$V_+ = 5V \Rightarrow \frac{15}{670k + R} \cdot R = 5$$

$$\Rightarrow R = 235k\Omega$$


Örnek-3:

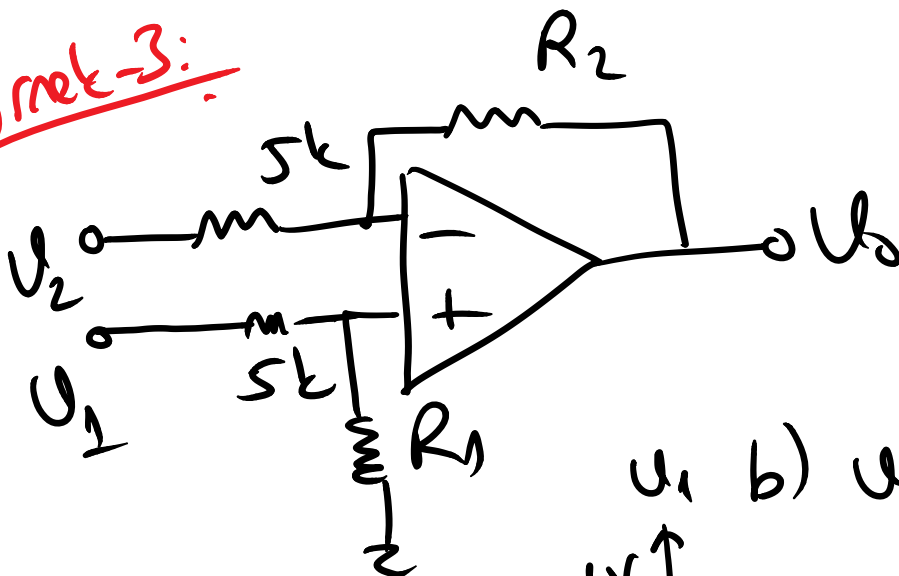

$$a) U_0 = 2U_1 - 3U_2$$


$$R_1 = ? \quad R_2 = ?$$

$$b) U_0 = ? \text{ a.c.}$$

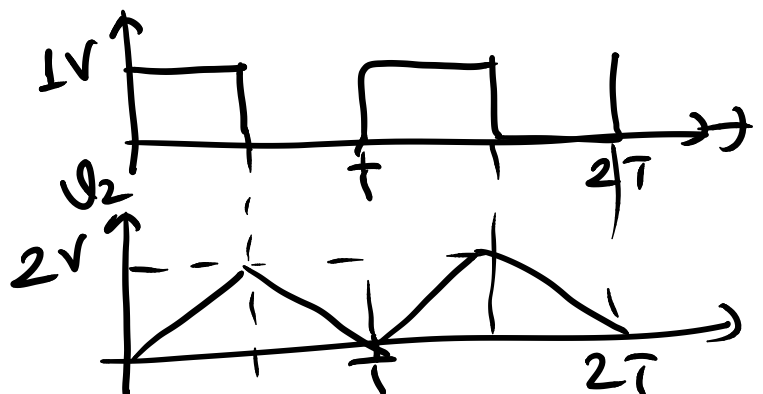

a) süperpozisyon.

⊛ U_1 'nin etkisi ($U_2 = 0V$)

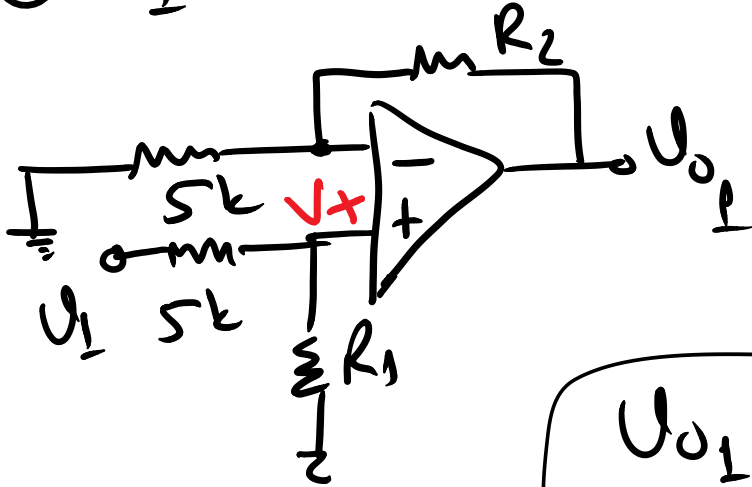


$$U_{o1} = \left(1 + \frac{R_2}{5k}\right) \cdot V_+$$

$$V_+ = \frac{U_1}{5k + 5k} \cdot R_1$$

$$U_{o1} = \frac{5k + R_2}{5k} \cdot \frac{R_1}{5k + R_1} \cdot U_1$$

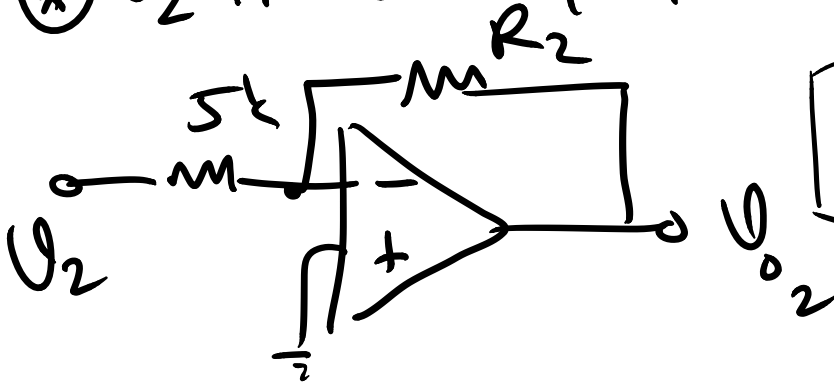⊛ U_2 'nin etkisi ($U_1 = 0V \Rightarrow V_+ = 0V$)



$$U_{o2} = -\frac{R_2}{5k} \cdot U_2$$


$U_o = 2U_1 - 3U_2$ old. göre;

$$-\frac{R_2}{5k} = -3 \Rightarrow R_2 = 15k\Omega$$


$$\frac{5k + R_2}{5k} \cdot \frac{R_1}{5k + R_1} = 2 \Rightarrow \frac{20k}{5k} \cdot \frac{R_1}{5k + R_1} = 2$$

$$4R_1 = 10k + 2R_1 \Rightarrow R_1 = 5k\Omega$$

b) $V_0 = 2V_1 - 3V_2$ 'y' a.r.

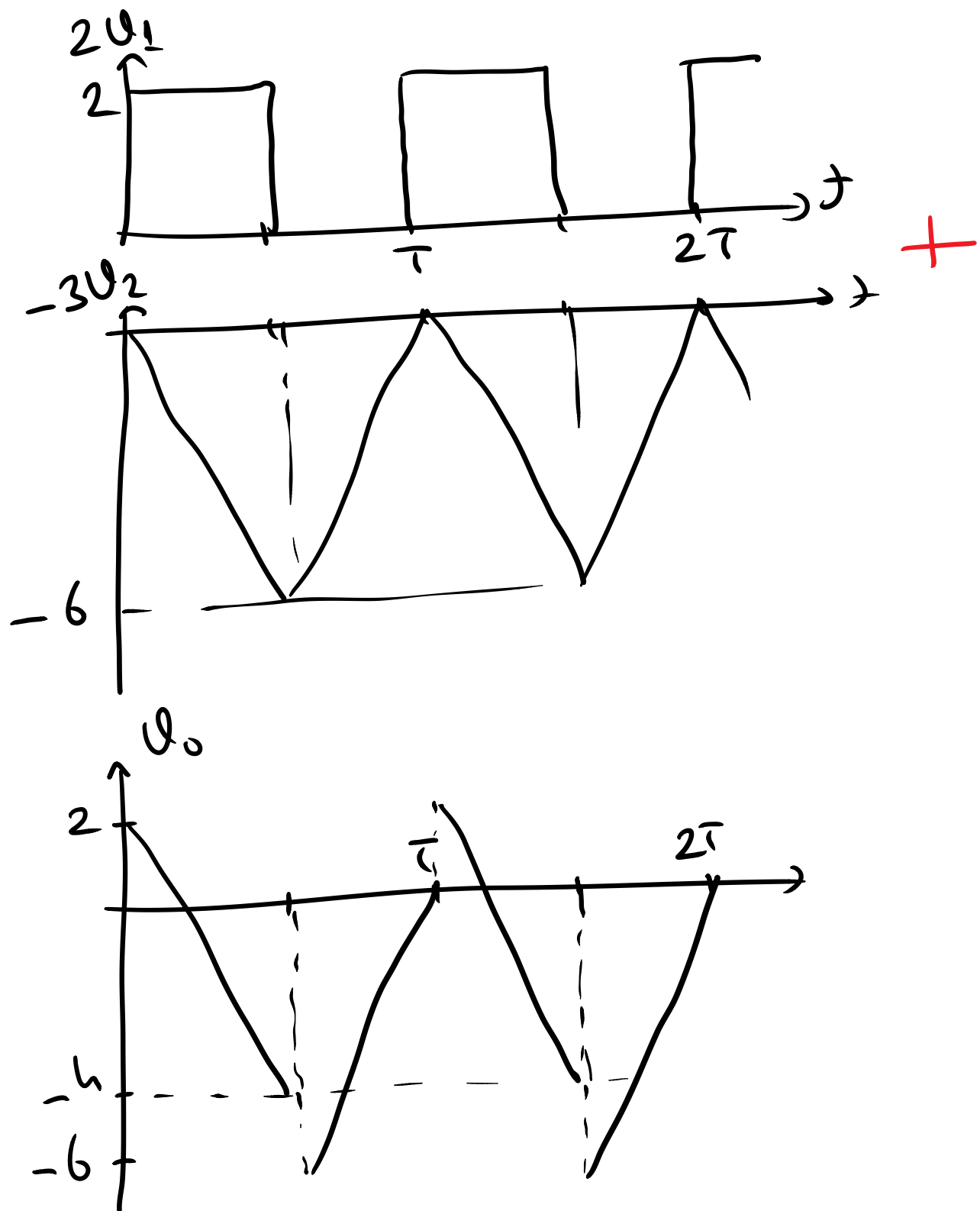

Örnek-4

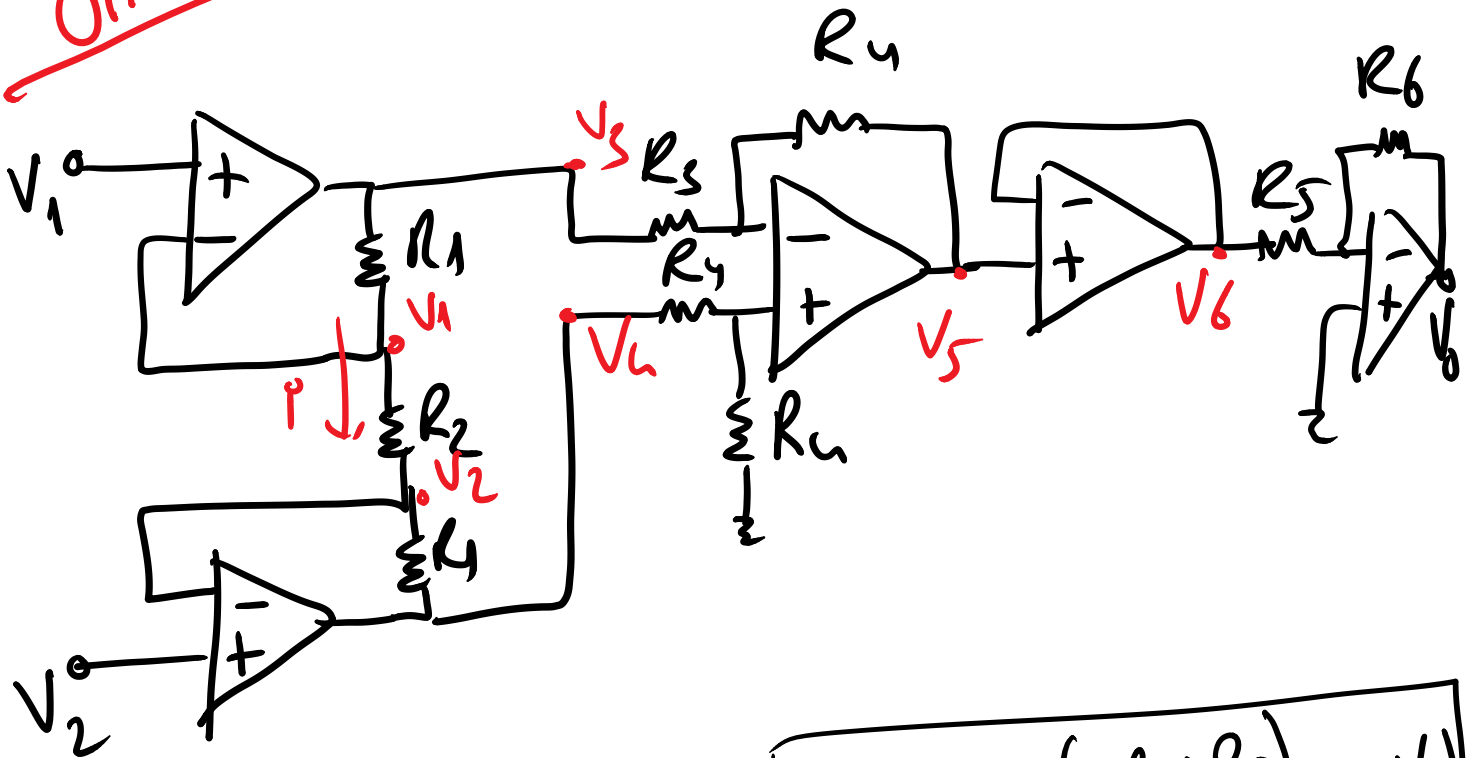

$$\frac{V_3 - V_4}{2R_1 + R_2} = \frac{V_1 - V_2}{R_2} \Rightarrow \boxed{V_3 - V_4 = \left(\frac{2R_1 + R_2}{R_2} \right) (V_1 - V_2)}$$


$$V_5 = -\frac{R_4}{R_3} (V_4 - V_3) \Rightarrow \boxed{V_5 = \frac{R_4}{R_3} (V_4 - V_3)}$$

$$\boxed{V_6 = V_5} \quad V_0 = -\frac{R_6}{R_5} \cdot V_6 = -\frac{R_6}{R_5} \cdot V_5$$

$$V_0 = \frac{R_6}{R_5} \cdot \frac{R_4}{R_3} (V_3 - V_4)$$

$$\boxed{V_0 = \frac{R_6 \cdot R_4 \cdot (2R_1 + R_2)}{R_5 \cdot R_3 \cdot R_2} (V_1 - V_2)}$$

Örnek-5:

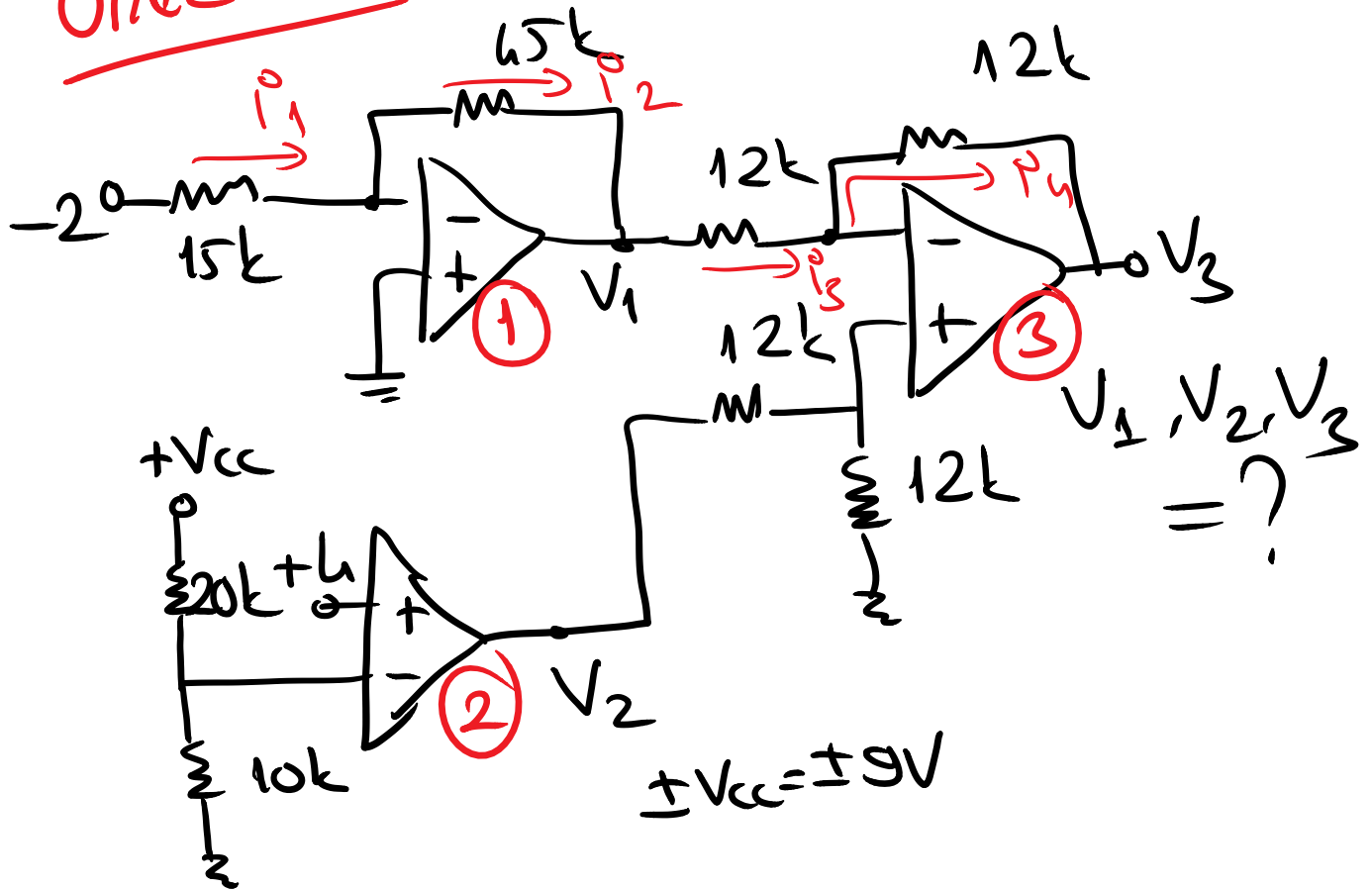

1. op-amp'ta:

$$V_1 = -\frac{65k}{15k} \cdot (-2) = 6V \Rightarrow \boxed{V_1 = 6V}$$


2. op-amp'ta: (kuvvetlendirici)

$$V_- = \frac{9}{30k} \cdot 10k = 3V, \quad V_+ = 6V \Rightarrow \boxed{V_2 = 9V}$$

3. op-amp'ta (cikarma devresi)

$$V_3 = \frac{12k}{12k} (V_2 - V_1) = 9 - 6V = 3V \Rightarrow \boxed{V_3 = 3V}$$

Örnek-6:

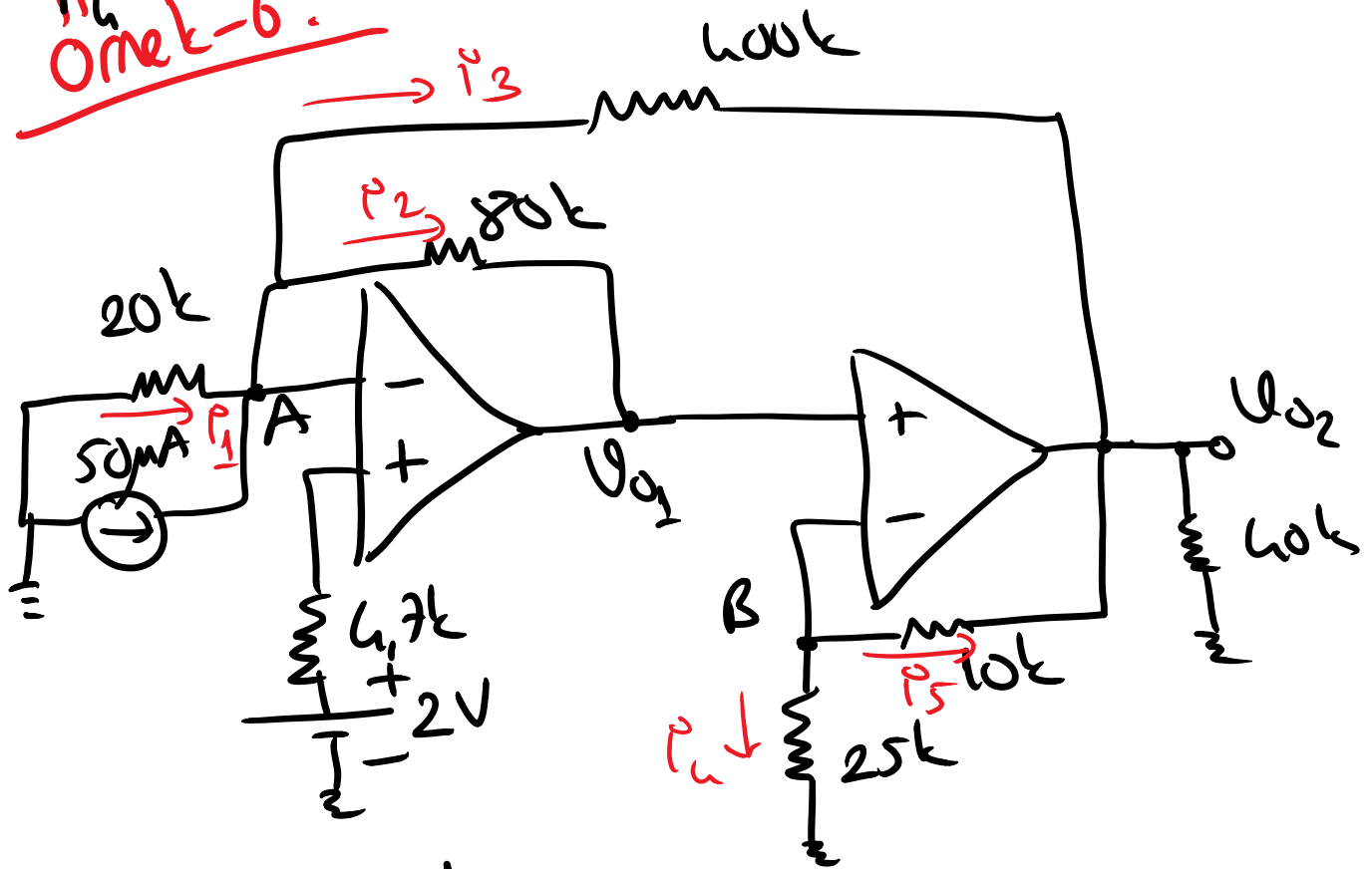

A noktasında:

$$i_1 + 50\mu A = i_2 + i_3$$

$$V_- = V_+ = 2V$$

$$\frac{-2}{20k} + 50\mu = \frac{2 - V_{01}}{80k} + \frac{2 - V_{02}}{400k}$$

$$50\mu - 100\mu = \frac{10 - 5V_{01}}{400k} + \frac{2 - V_{02}}{400k}$$

$$-50\mu \cdot 400k = 10 - 5V_{01} - V_{02}$$

$$5V_{01} + V_{02} = 32 \quad (1)$$

B noktasında:

$$I_4 + I_5 = 0 \quad V_+ = V_- = U_{01}$$

$$\frac{U_{01}}{25k} + \frac{U_{01} - U_{02}}{10k} = 0$$

$$\frac{2U_{01} + 5U_{01} - 5U_{02}}{50k} = 0$$

$$\Rightarrow 7U_{01} = 5U_{02} \Rightarrow \boxed{U_{02} = \frac{7}{5}U_{01}} \quad \dots (2)$$


(2) nolu ifadeyi (1) nolu denkleme yerine yazarak:


$$5U_{01} + \frac{7}{5}U_{01} = 32$$

$$\frac{25U_{01} + 7U_{01}}{5} = 32 \Rightarrow \frac{32}{5}U_{01} = 32$$

$$\boxed{U_{01} = 5V} \quad \boxed{U_{02} = 7V}$$

Örnek - 7:

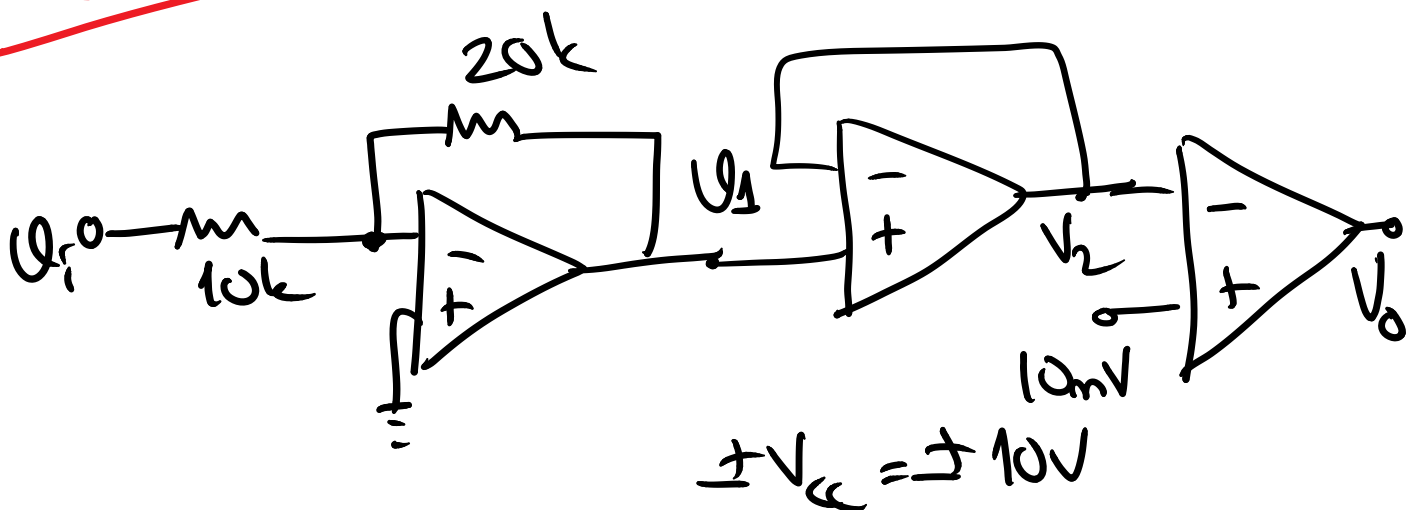

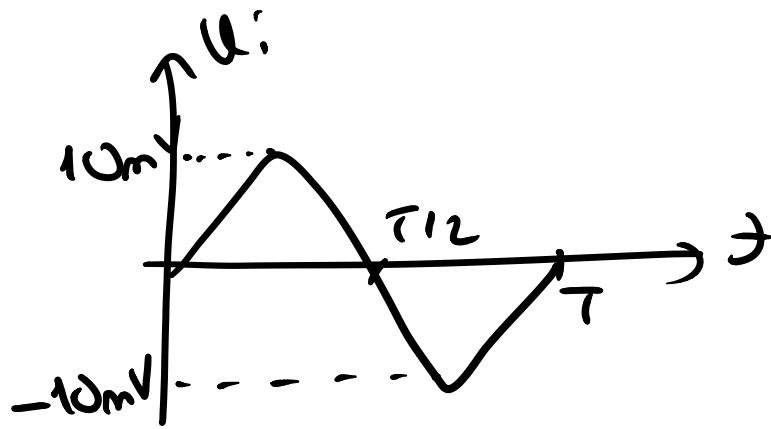

$$V_1, V_2, V_o = ?$$

Ci2.

$$V_1 = -\frac{20\text{k}}{10\text{k}} \cdot u_i \Rightarrow \underline{\underline{V_1 = -2u_i}}$$

$$\underline{\underline{V_2 = V_1}}$$

$$V_o = \begin{cases} +10 & V_2 < 10\text{mV} \text{ ise} \\ -10 & V_2 > 10\text{mV} \text{ ise} \end{cases}$$

