
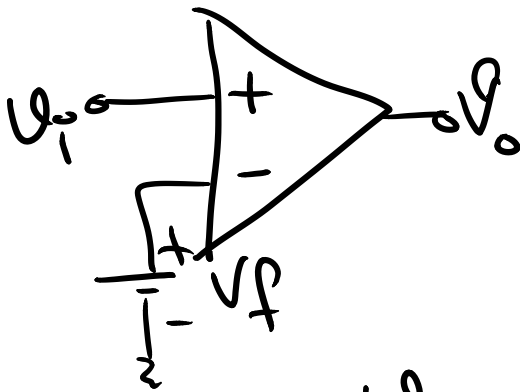



Schmitt Tetikleyici :

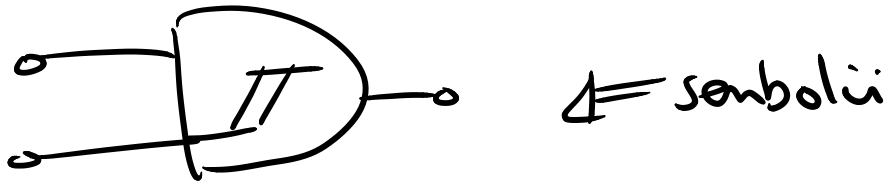



V_o :

$U_i > V_T$ ise $+V_{CC}$


$U_i < V_T$ ise $-V_{CC}$

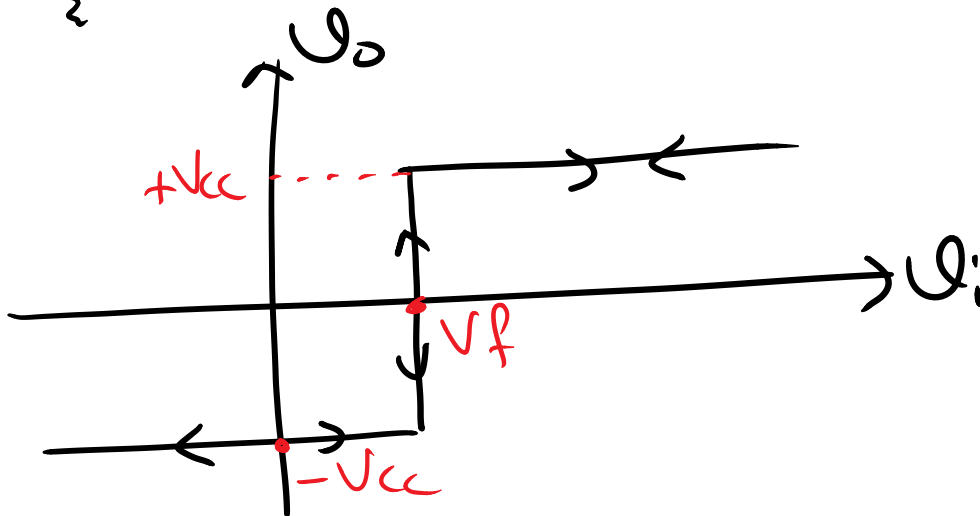

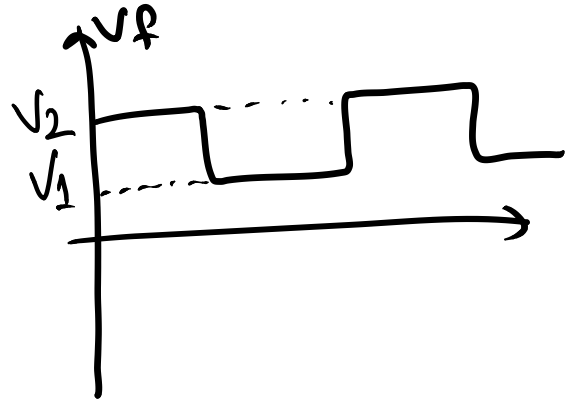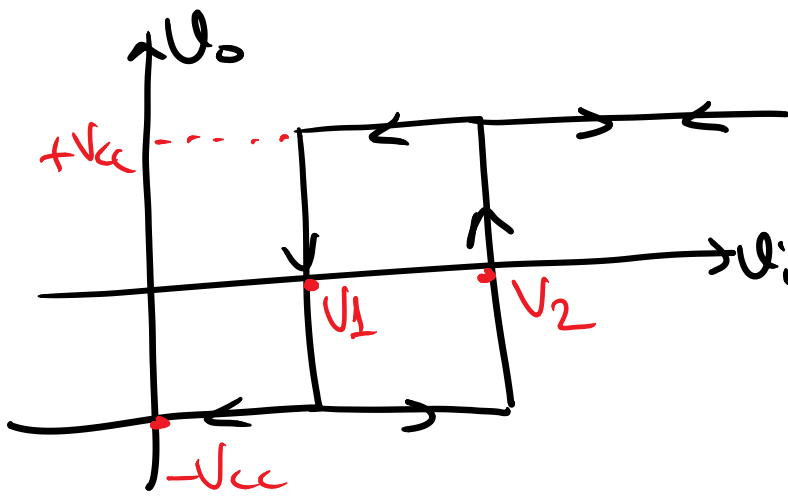Eğer V_T 'i $[V_1 - V_2]$ gibi bir aralıkta
değiştirsek:



Örnek:

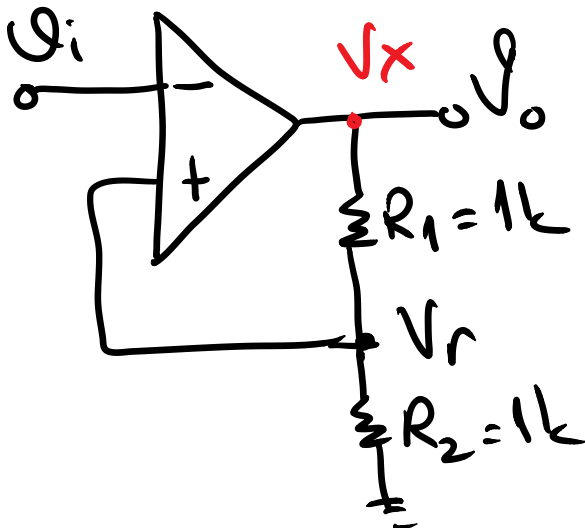

$$V_r = \frac{V_x}{R_1 + R_2} \cdot R_2$$

⊗ $V_x = +V_{cc}$ ise

$$V_r = \frac{V_{cc} \cdot 1k}{2k}$$

$$V_r = \frac{V_{cc}}{2}$$

$U_i > V_r$ iken $V_x = -V_{cc}$ ⊗ $V_x = -V_{cc}$ ise
 $U_i < V_r$ iken $V_x = +V_{cc}$ $V_r = -\frac{V_{cc}}{2}$

Örneğin $\pm V_{cc} = \pm 10V$ ise $\Rightarrow V_r = \pm 5V$

