


$$\frac{11}{1.26} =$$

Adı Soyadı : SERHAT DALBAS

$$\frac{11}{1.26} = 8.73$$

$$\frac{V_i}{1.26} = 8.73$$

S.1-

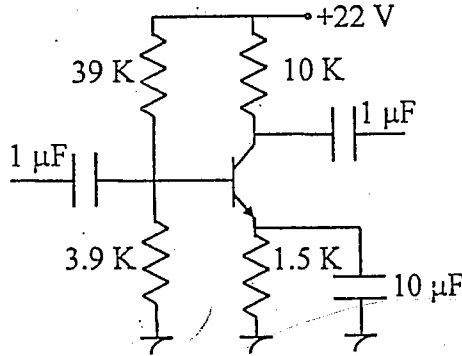


$$h_{ie} = 1.2 \text{ K}, h_{fe} = 70$$


$$Z_i = ?, Z_o = ?, A_v = ?, A_i = ?$$

$$\frac{70 \times 1.2}{1.26} = 65.9$$

$$52.318$$

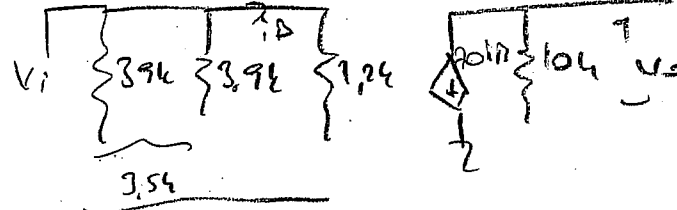

S.2-

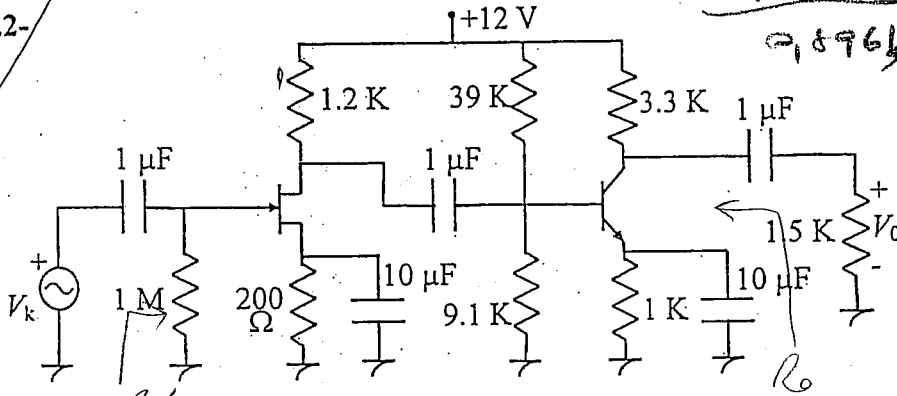


$$h_{ie} = 2 \text{ K}, h_{fe} = 120, g_m = 3 \text{ mS}$$

$$R_i = ?, R_o = ?$$

$$\frac{V_o}{V_k} = ?$$


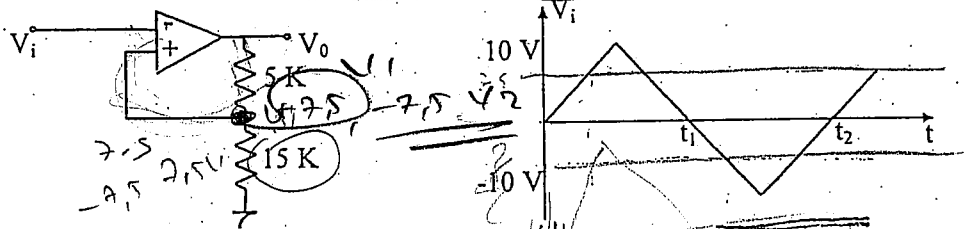
S.3- V_o 'ın değişimini V_i ile alt alta çiziniz ($V_{cc} = \pm 10 \text{ Volt}$).



$$A_i = \frac{V_o}{V_i} = 0.75$$

$$A_v = \frac{V_o}{V_k} = 0.75$$

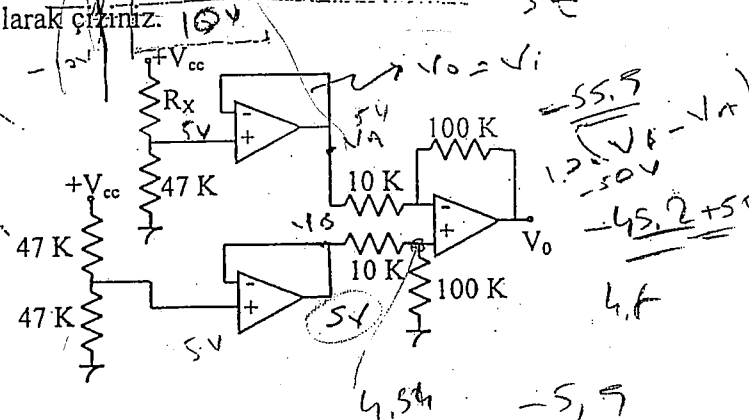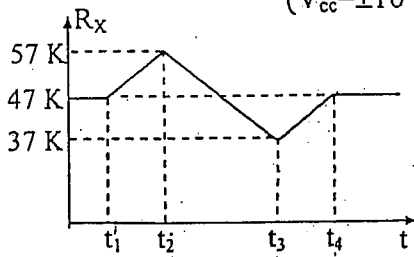S.4- V_o 'ın zamana göre değişimini ölçekli olarak çiziniz. ($V_{cc} = \pm 10 \text{ Volt}$)



Not: Sınav süresi 90 dakikadır. Sorular eşit puanlıdır.

Başarılar dilerim.

Doç. Dr. Saadetdin HERDEM

