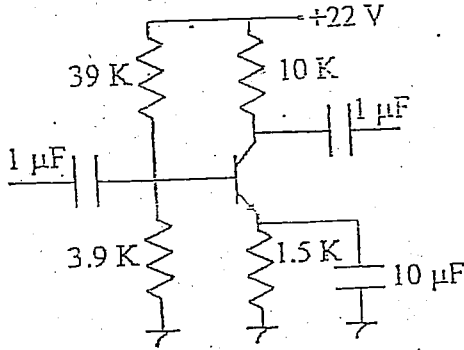


Adı Soyadı : İlhan ÜNLÜ

S2)





$h_{ie} = 1.2 \text{ K}$, $h_{fe} = 70$

$Z_i = ?$, $Z_o = ?$, $A_v = ?$, $A_f = ?$

0.932 , $10K$, -583.33 , 1972 , $S2$

S2)

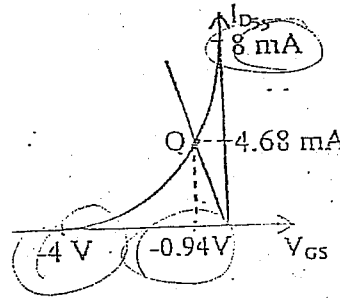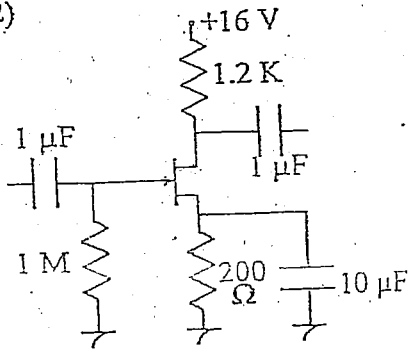

$Z_i = ?$, $Z_o = ?$, $A_v = ?$

$1M$, -3.672

$1.2K$

$-3m$

$\frac{2}{10K} = \frac{V_1 - ?}{47K}$

$V_E = 2$

$\frac{2-0}{10K} = \frac{V_2-0}{57K}$

$V_{CC} = \pm 15 \text{ Volt}$

$V_1 = ?$, $V_2 = ?$, $I_x = ?$

2 , 11.4 , $5138mA$

$V_{CC} = \pm 5 \text{ Volt}$

$V_1 = +2 \text{ V}$, $V_2 = +1 \text{ V}$

$V_3 = ?$, $V_4 = ?$, $V_5 = ?$

$-5V$, 0 , $4V$

$\frac{2}{10K} = \frac{V_2 - 2}{47K}$

$11.4 = V_2$

$\frac{11.4}{57K} + \frac{11.4}{20K} = I_x$

Not: Sınav süresi 60 dakikadır. Sorular eşit puanlıdır. Başarılar dilerim.

Doç. Dr. Saadetdin HERDEM

$\frac{V_2}{57K} = \frac{10V}{57K} = V_1$
 $V_2 = 5.74V$

$51703 = 11.4$